

Lecture 12:

Memory (SRAM, DRAM, Flash)

Jangwoo Kim (Seoul National University)

jangwoo@snu.ac.kr

Read-Only Memories

- ◆ Mask ROM
 - Programmed permanently during manufacturing process
- ◆ Programmable ROM
 - PROM
 - programmed by fusing or anti-fusing process
 - the process is irreversible
 - Erasable PROM
 - UV EPROM
 - EEPROM

Random Access Memories

- ◆ Transistor efficient methods for implementing storage elements
- ◆ Small RAM: 256 words by 4-bit
- ◆ Large RAM: 1 billion words by 1-bit
- ◆ Static RAMs and Dynamic RAMs

SRAM

(Static Random Access Memory)

Static RAM (SRAM) (1/2)

◆ Static Random Access Memory


- Cache
- Register file
- ...

◆ Read

- Sense bitline difference


◆ Write

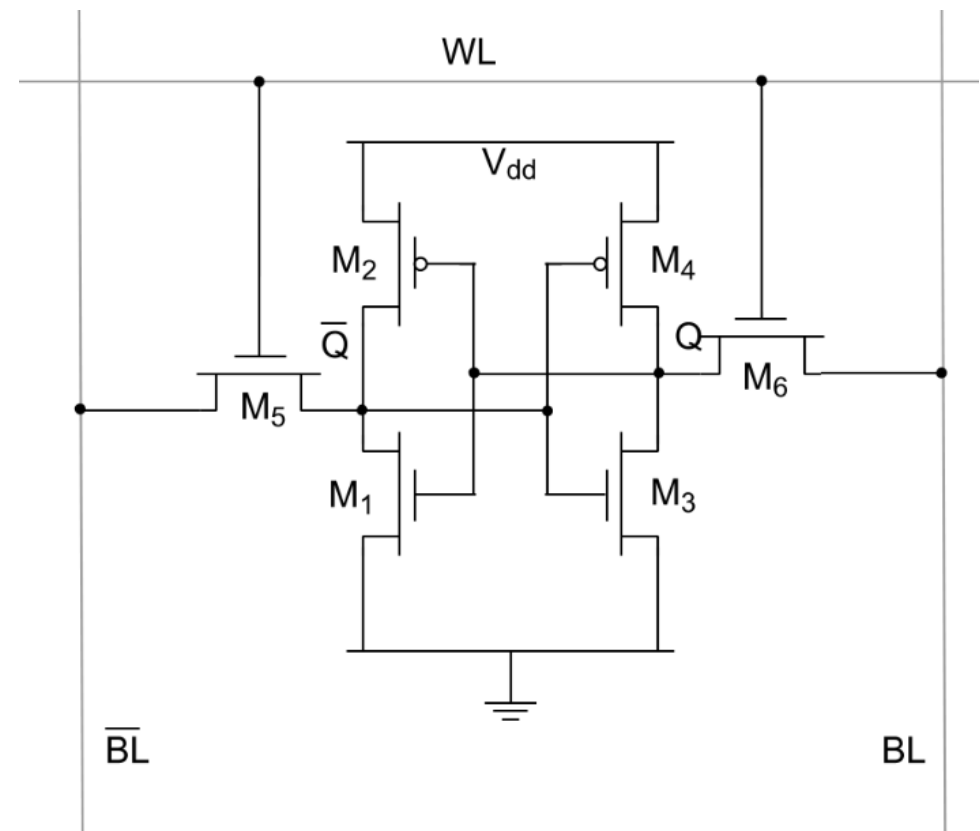- Overwrite bitlines using strong signals



1 Cell = 6 transistors (typical) 4 (two invertors) + 2 (switches)

Static RAM (SRAM) (2/2)

 

Read Sequence

(assume bitlines are precharged)

1. Address decode
2. Drive row select
3. Selected bit-cells drive bitlines
(entire row is read together)
4. Diff. sensing and column select
(data is ready)
5. Precharge all bitlines
(for next read or write)


How do you write select columns?

Access latency dominated by steps 2, 3

Cycle time dominated by steps 2, 3, 5

- Step 2 proportional to 2^m
- Step 3 and 5 proportional to 2^n

 usually encapsulated by synchronous
(sometime pipelined) interface logic



Static RAMs



- ◆ We will discuss a 1024 x 4 organization

Chip Select Line (active lo)

Write Enable Line (active lo)


10 Address Lines

4 Bidirectional Data Lines

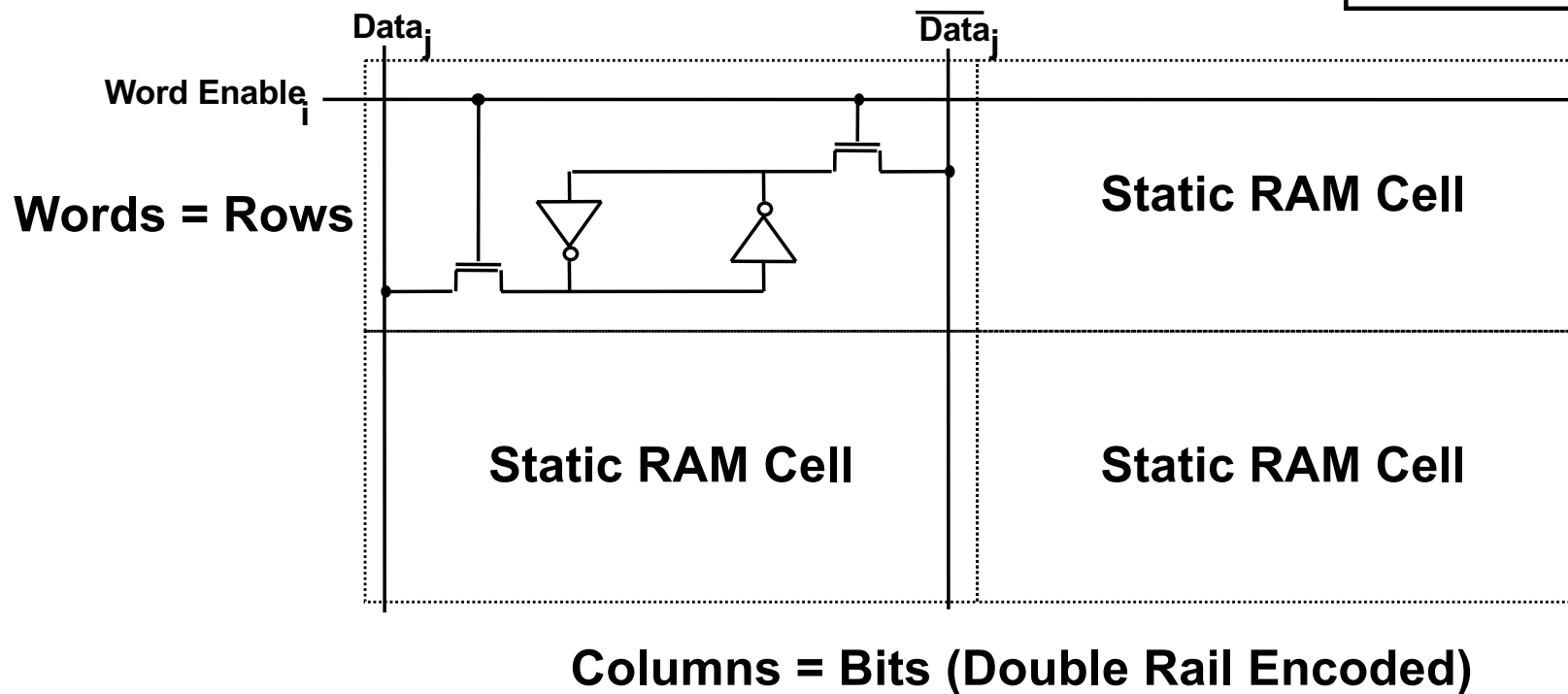 

RAM Organization

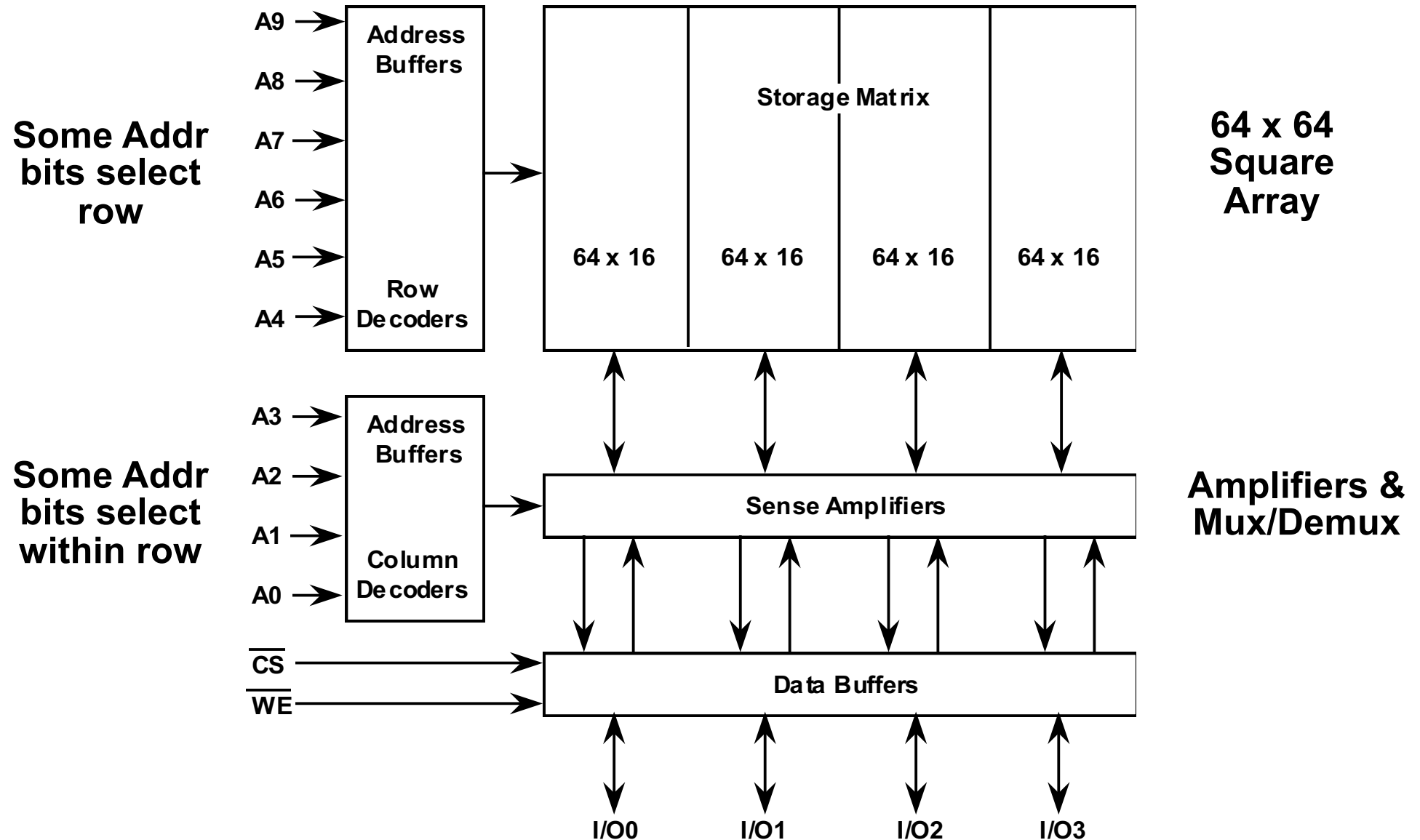Long thin layouts are not the best organization for a RAM







Static RAMs

RAM Timing

Simplified Read Timing

 


Simplified Write Timing

 


DRAM

(Dynamic Random Access Memory)

 

Dynamic RAMs

 

1 Transistor (+ capacitor) memory element

Read: Assert Word Line, Sense Bit Line


Write: Drive Bit Line, Assert Word Line

Need for Refresh Cycles: storage decay in ms

Destructive Read-Out

Internal circuits read word and write back

Dynamic RAM (DRAM)

 

Bits stored as charge in capacitor

- Precharge bitline to $V_{dd}/2$
 - Bit cell loses charge when read
 - Bit line charge increases
 - Bit cell drains over time
 - Bit line charge decreases


*** Disruptive Read!!**

Requires periodic refresh

- Performed by mem controller
- Refresh interval 10's of ms
- DRAM unavailable during refresh

Basics: DRAM organization

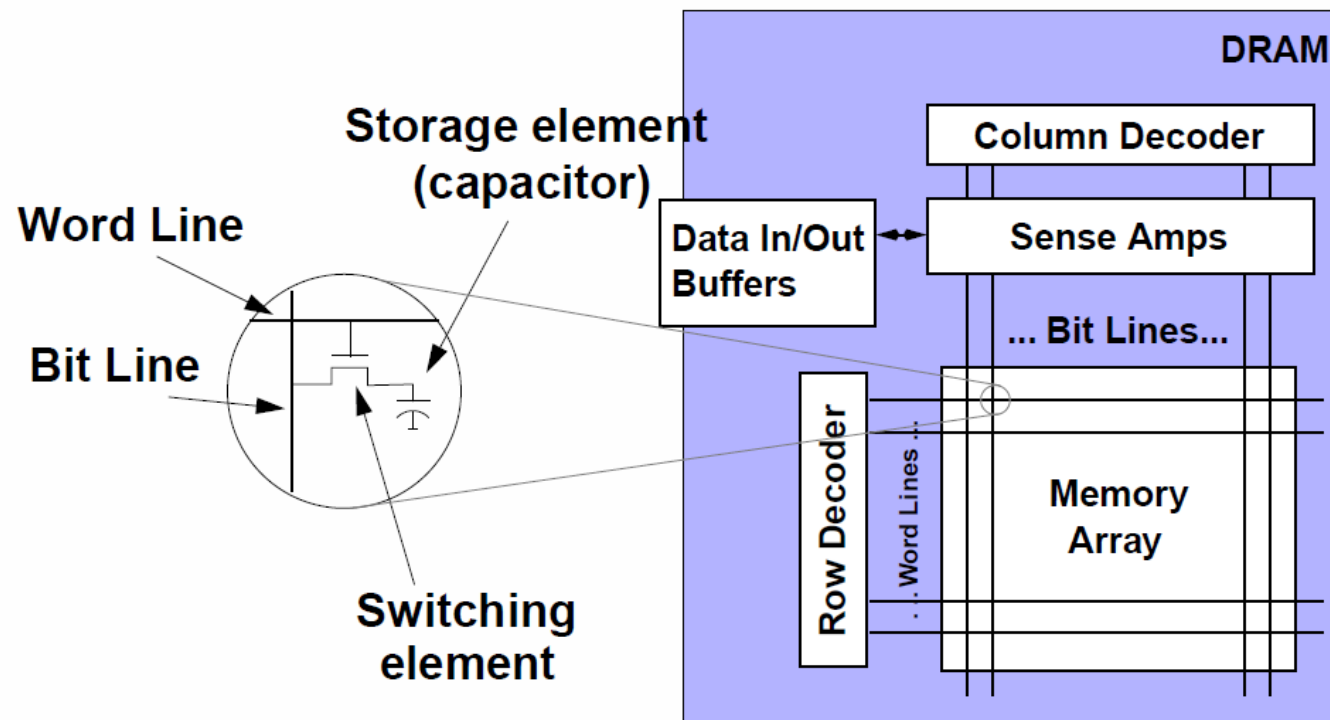
- ◆ One bit = One Capacitor
- ◆ Accessed by Word Line (row) and Bit Line (column)






Basics: Access Process (1/5)

(1) BUS TRANSMISSION

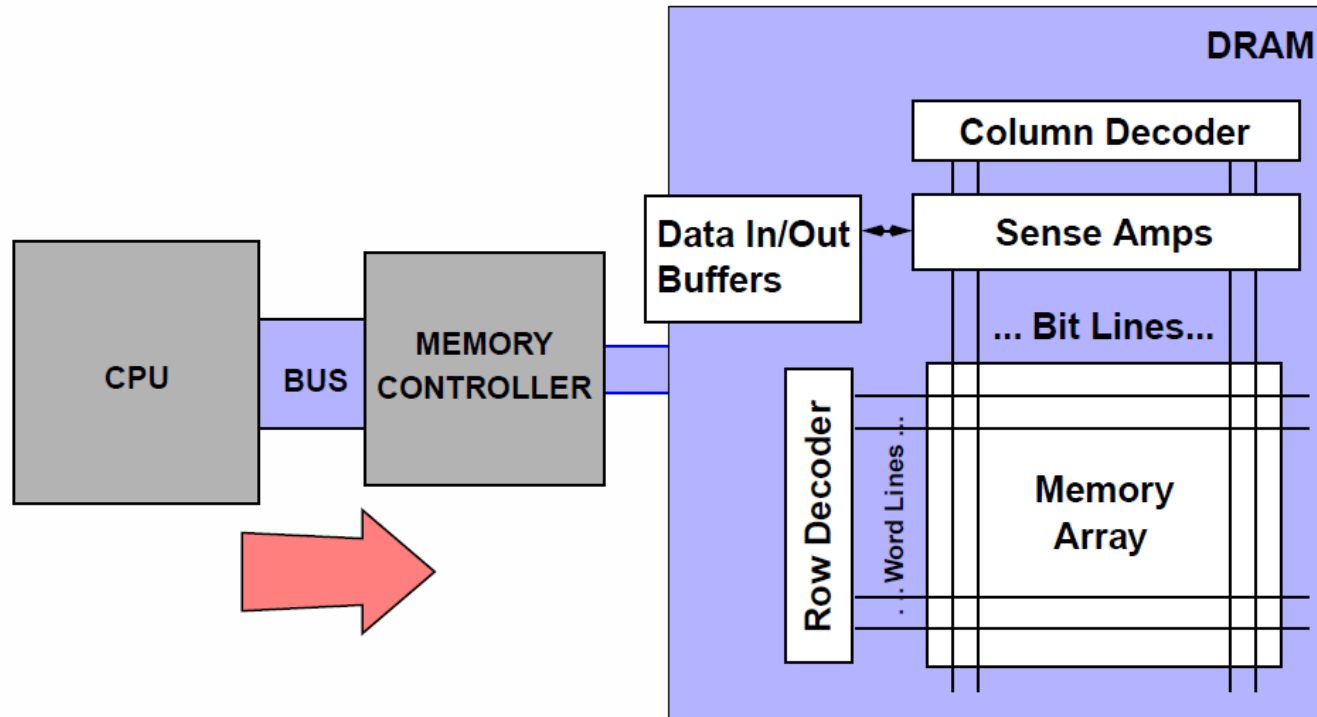

Basics: Access Process (2/5)


(2) (optional PRECHARGE) & ROW ACCESS

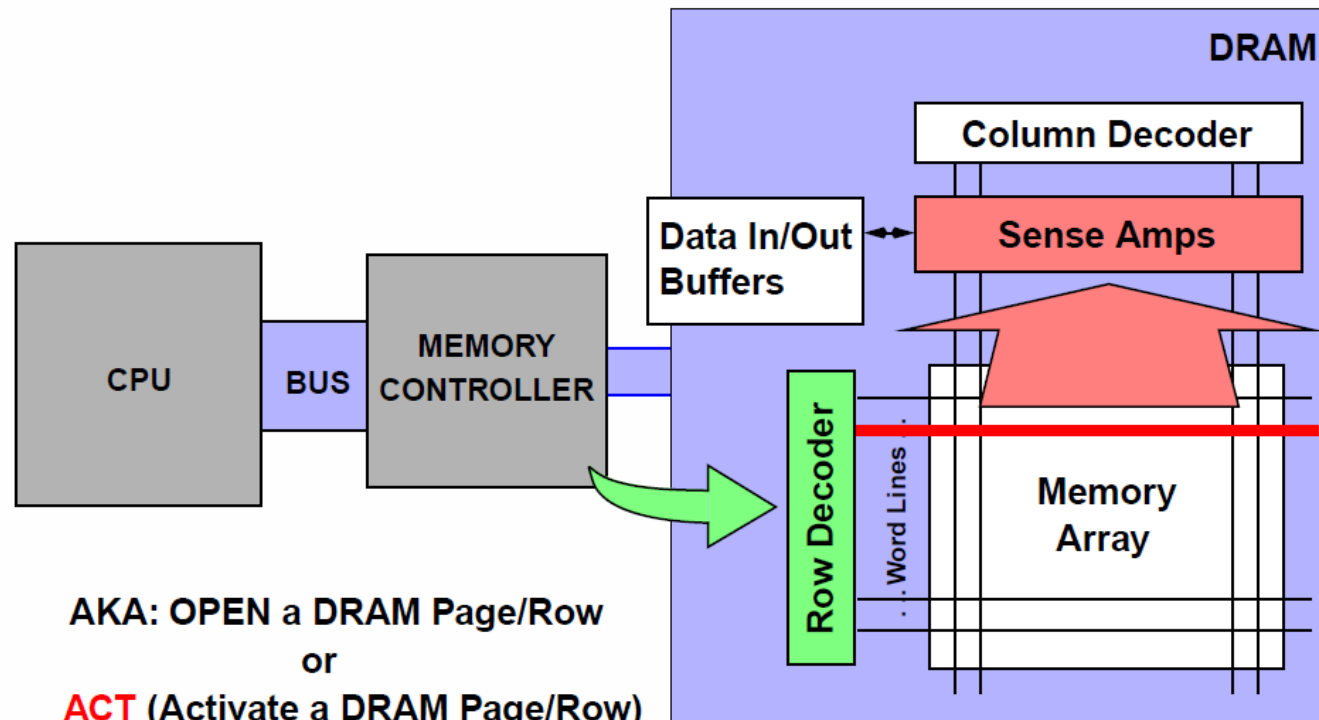

AKA: OPEN a DRAM Page/Row
or
ACT (Activate a DRAM Page/Row)
or
RAS (Row Address Strobe)


Basics: Access Process (3/5)

(3) COLUMN ACCESS

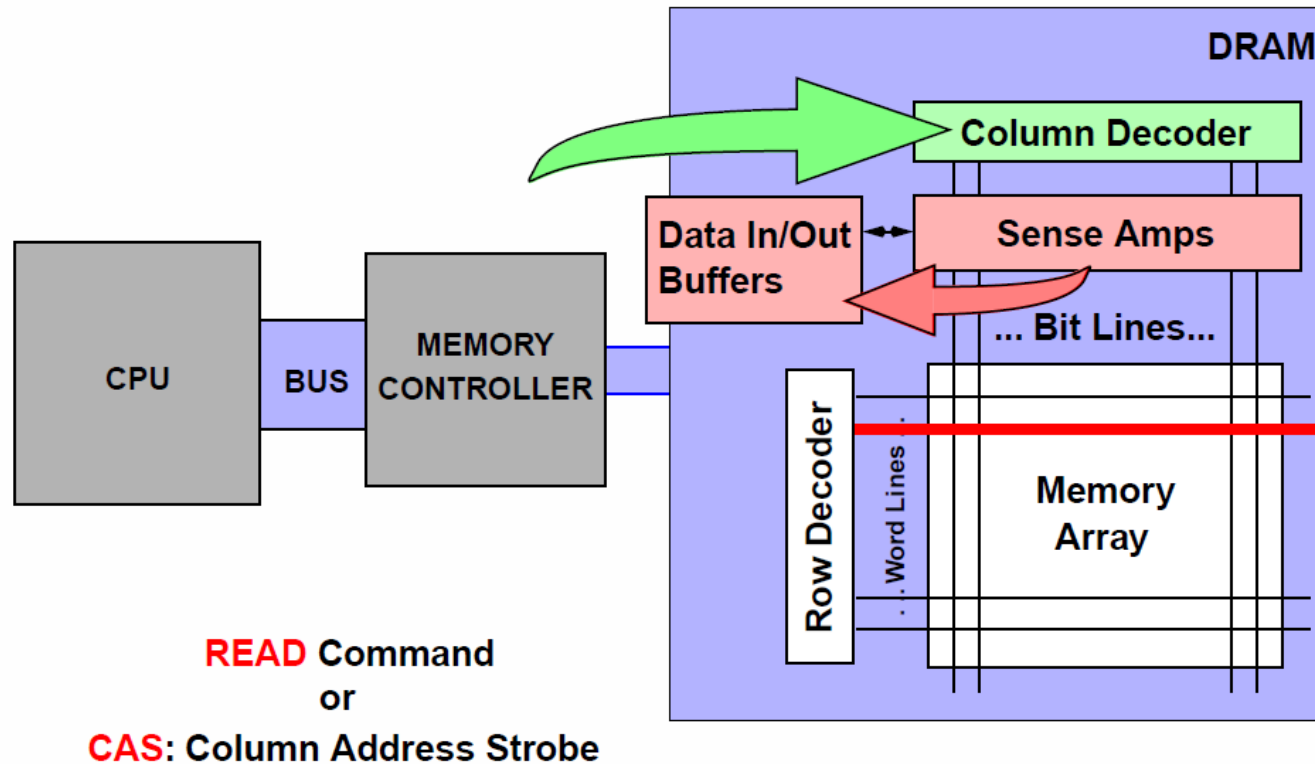


Basics: Access Process (4/5)

(4) DATA TRANSFER

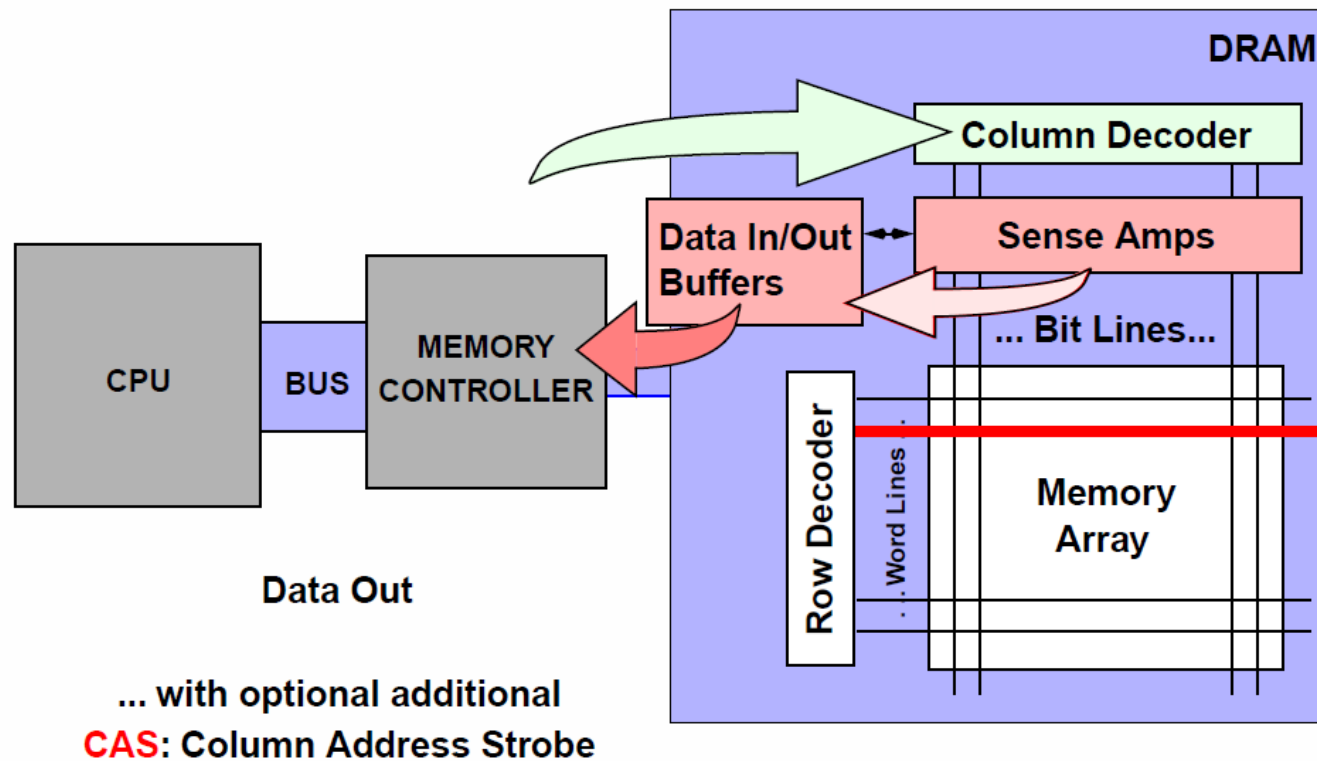


Basics: Access Process (5/5)

(5) BUS TRANSMISSION

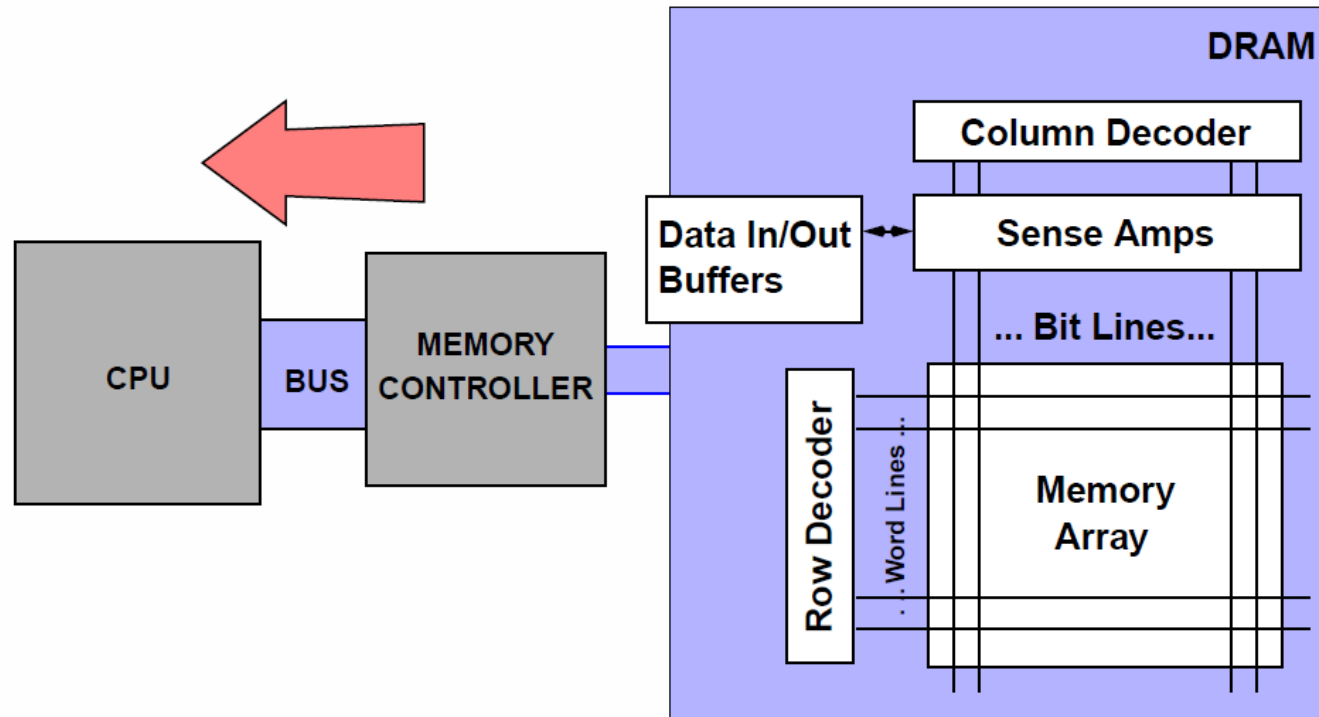

DRAM Latency

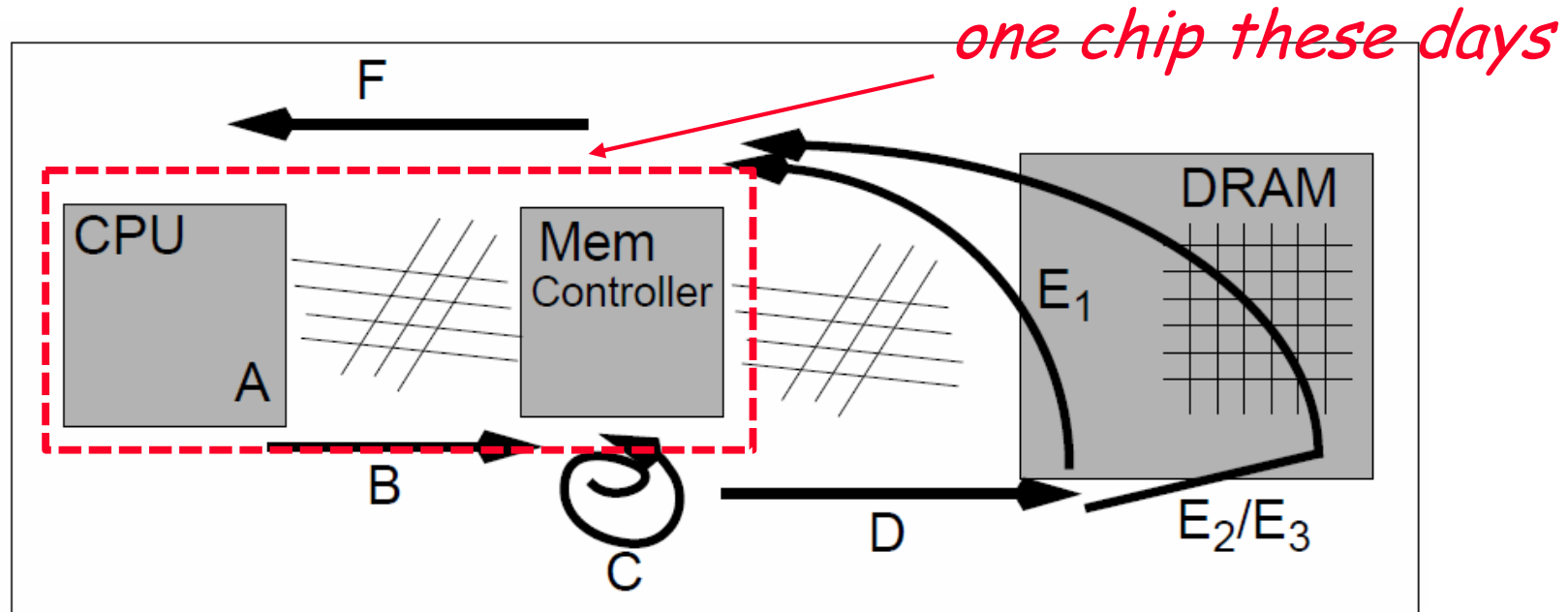

◆ $\text{DRAM Latency} = A + B + C + D + E + F$

A: Transaction request may be delayed in queue

B: Transaction request sent to memory controller

C: Transaction request converted as DRAM command sequences

D: Commands sent to DRAM

E: Access DRAM : E1 (CAS) or E2 (RAS+CAS) or E3 (PRE+RAS+CAS)

F: Transaction sent back to CPU

Dynamic RAMs

DRAM Organization


Long rows to simplify refresh

Two new signals: RAS, CAS

Row Address Strobe

Column Address Strobe

Replace Chip Select

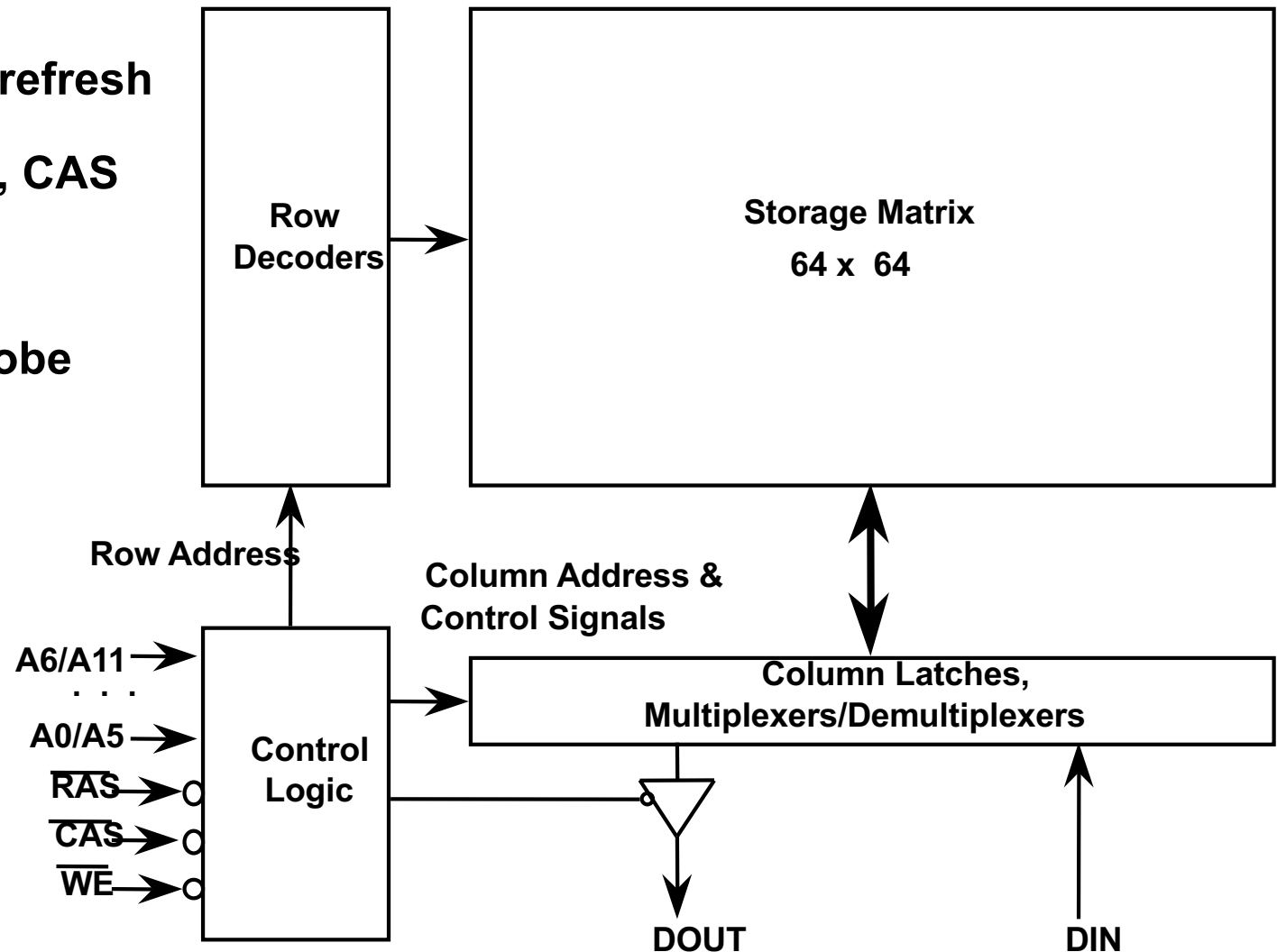


Dynamic RAMs

RAS, CAS Addressing


Even to read 1 bit, an entire 64-bit row is read!

 Separate addressing into two cycles: Row Address, Column Address
Saves on package pins, speeds RAM access for sequential bits!



Dynamic RAMs

Write Cycle Timing

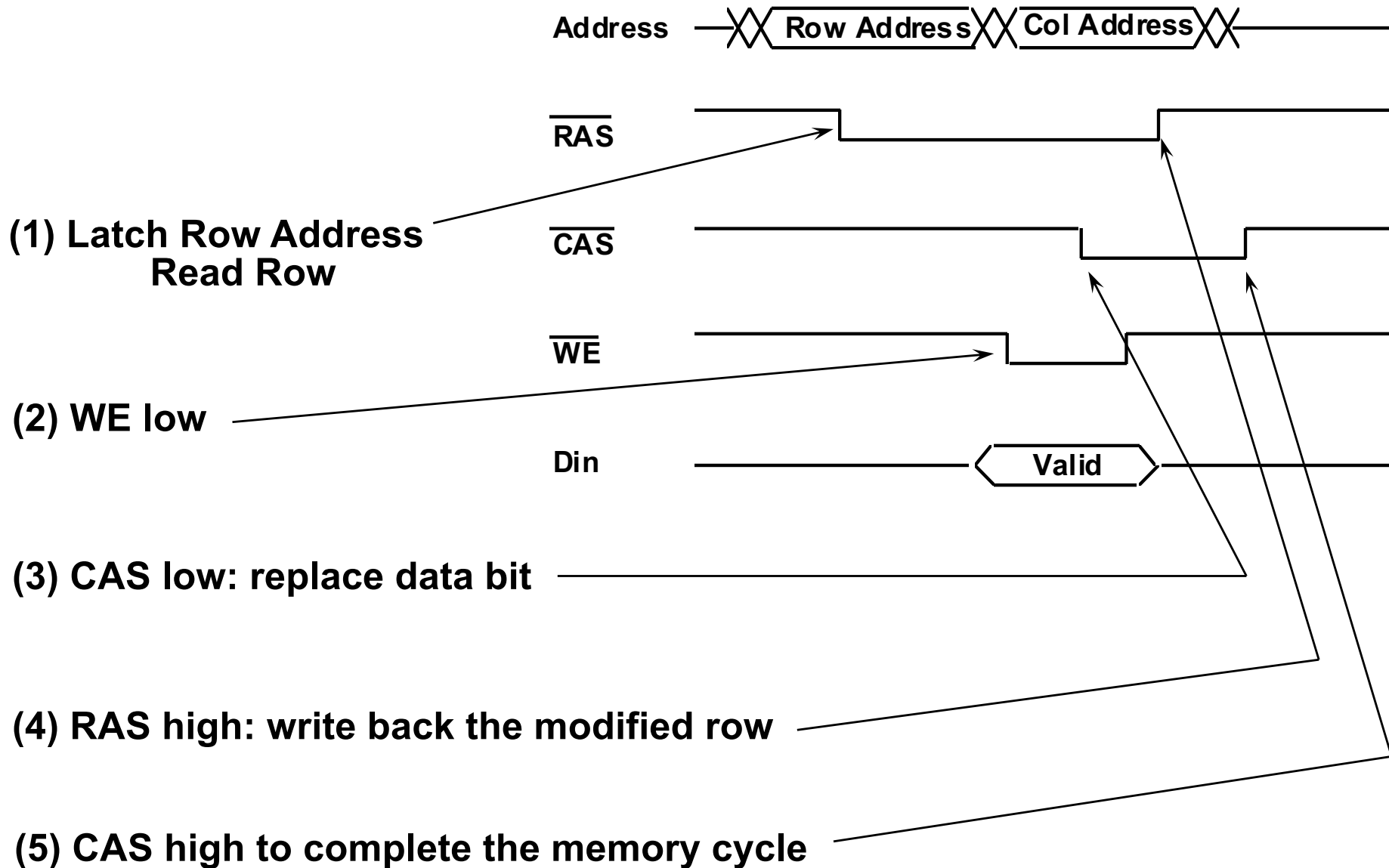

Dynamic RAMs

RAM Refresh

Refresh Frequency:

4096 word RAM -- refresh each word once every 4 ms
→ This is one refresh cycle every 976 ns

Assume 120ns memory access cycle
→ 1 in 8 DRAM accesses

But, RAM can be organized into 64 rows (with a row refresh)
→ This is one refresh cycle every 62.5 μ s
→ 1 in 500 DRAM accesses

Large capacity DRAMs have 256 rows, refresh once every 16 μ s

RAS-only Refresh (RAS cycling, no CAS cycling)

External controller remembers last refreshed row

“CAS before RAS” signaling

If CAS goes low before RAS, then do refresh

Dynamic RAMs

◆ DRAM Variations

Page Mode DRAM:

Can read/write a bit within the last accessed row without RAS cycle

RAS, CAS, CAS, . . ., CAS, RAS, CAS, ...

New column address for each CAS cycle

Static Column DRAM:

Similar to page mode, but address bit changes trigger column reads without using multiple CAS cycling

On writes, de-select chip or disable CAS while address changes

Nibble Mode DRAM:


Another variation of page mode.

CAS cycling implies “next column address” in sequence
-- no need to specify column address after first CAS

Works for 4 bits at a time (hence "nibble")


RAS, CAS, CAS, CAS, CAS, RAS, CAS, CAS, CAS, CAS, ...

Read Timing of Fast Page Mode

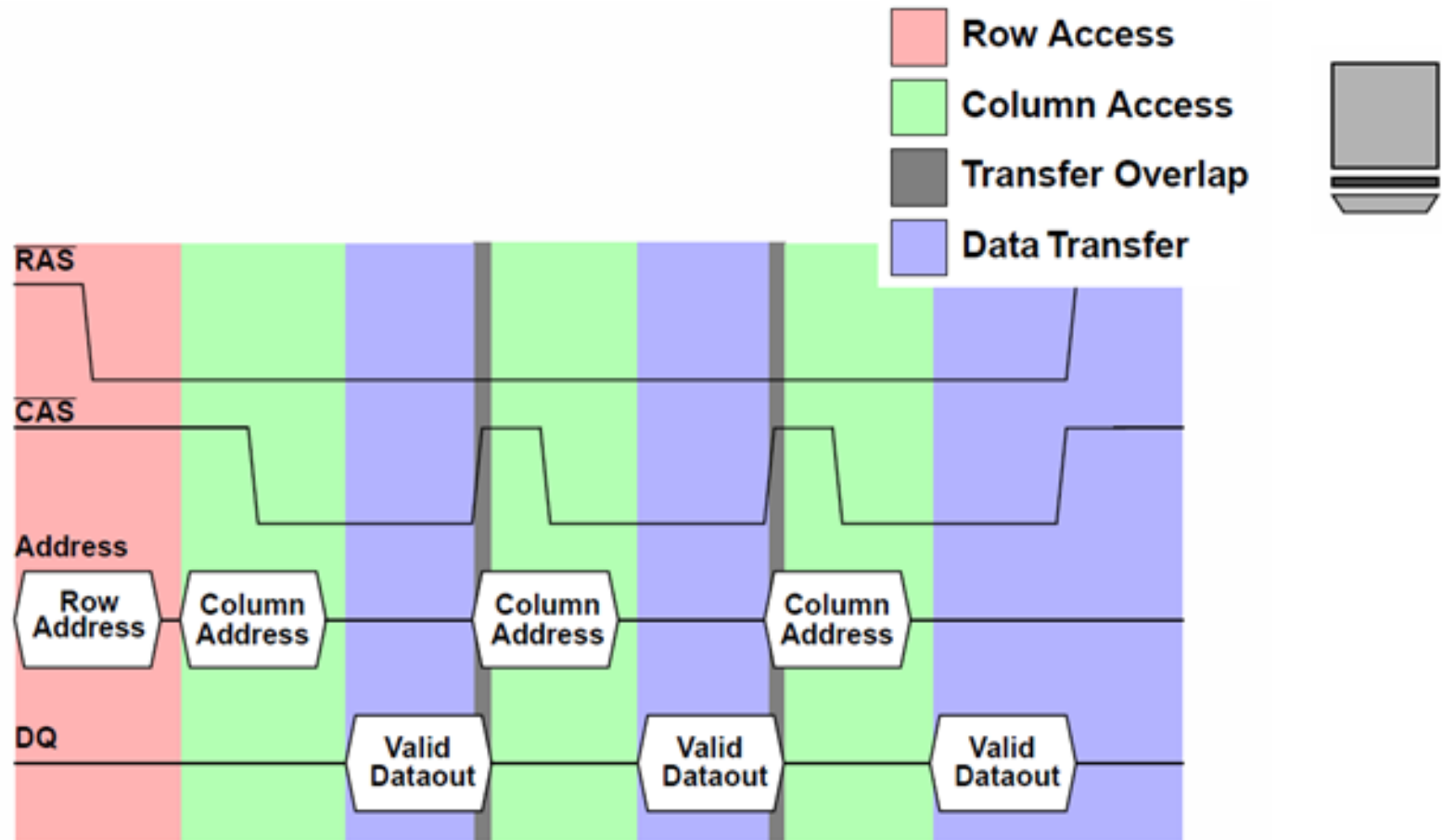

- One row address, multiple column addresses
- Exploits page buffering (or **Row Buffer**) that DRAMs already require internally

Read Timing of Burst (Nibble) Mode

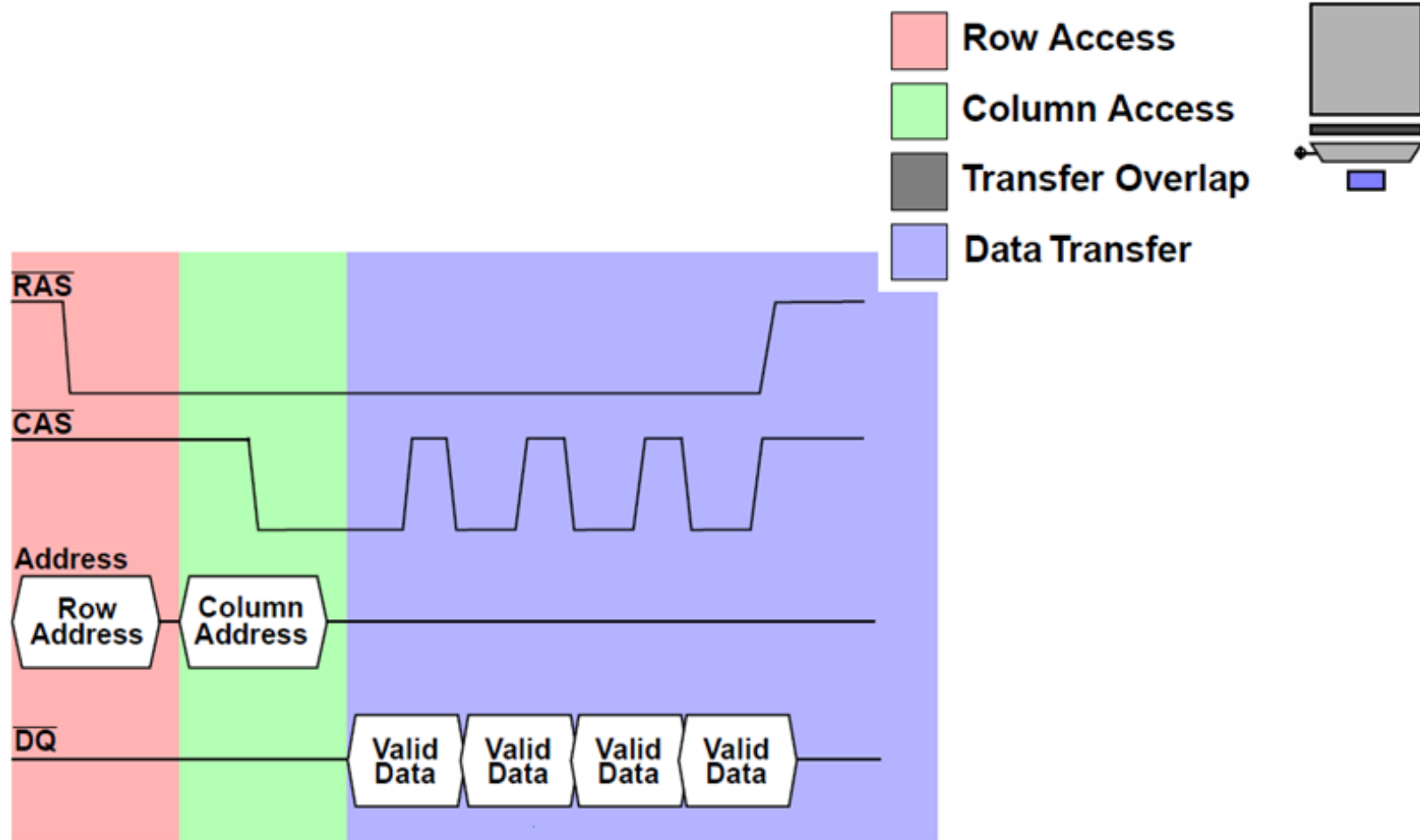


CAS Strobe indicates proceed to next sequential column address

Dynamic RAMs


- ◆ More advanced DRAM technologies
 - **EDO DRAM** (Extended Data Out DRAM)
 - One access to the memory can begin before the last one has finished
 - **SDRAM** (Synchronous DRAM)
 - Tied to the system clock and is designed to be able to read or write memory in burst mode (after the initial read or write latency) at 1 clock cycle per access (zero wait states)
 - **DDR SDRAM** (Double Data Rate SDRAM)
 - Doubles the bandwidth of the memory by transferring data twice per cycle on both the rising and falling edges of the clock signal
 - DDR2, DDR3, ...
 - **DRDRAM** (Direct Rambus DRAM)
 - **SLDRAM** (Synchronous-Link DRAM)

Read Timing of EDO Mode

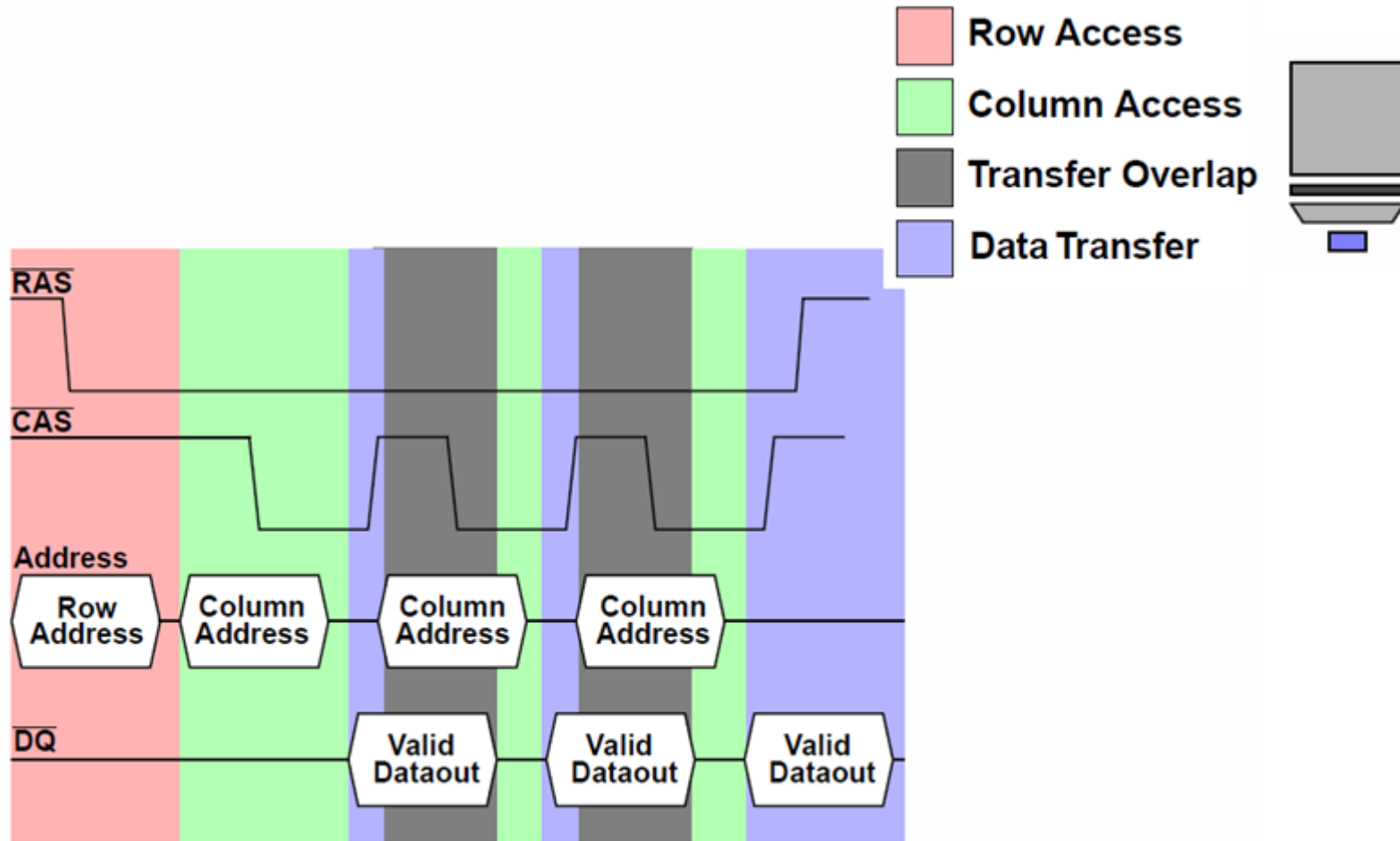


- As in FPM
- But overlapped Column Address assert with Data Out

Synchronous DRAM (SDRAM)

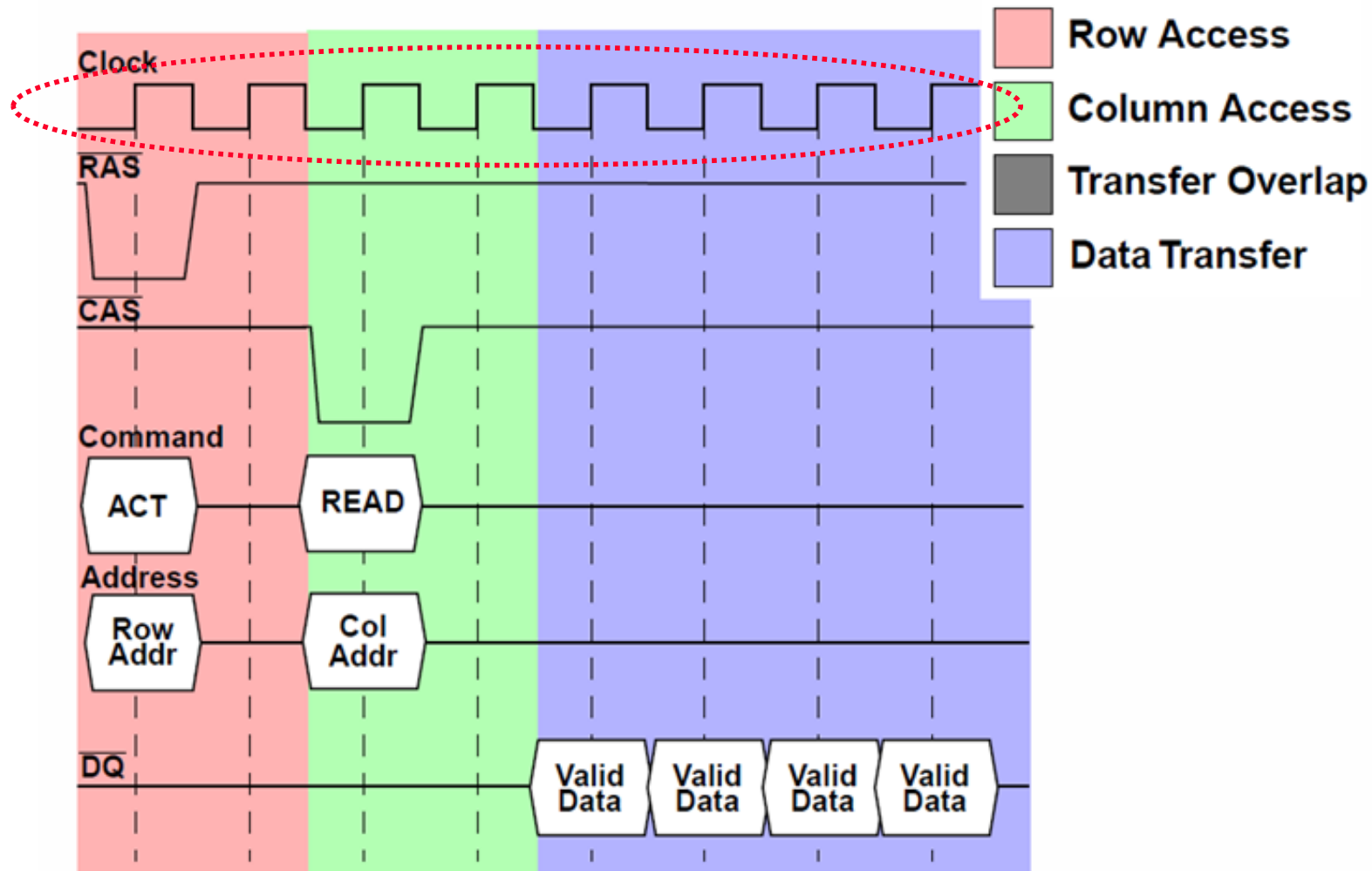


Adding a clock allows faster transfers


Basics: Physical Organization

 


ECC
(optional)

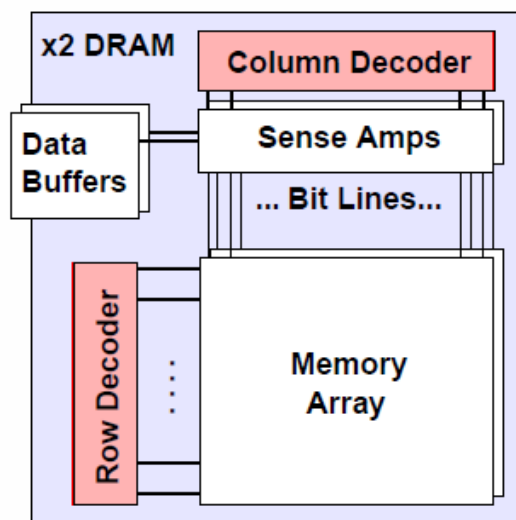

x2 DRAM

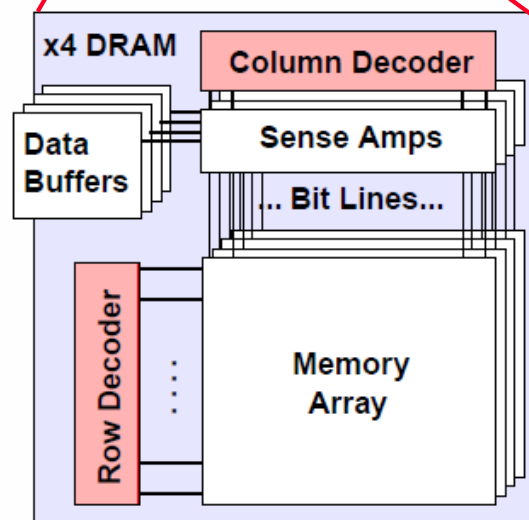

x4 DRAM

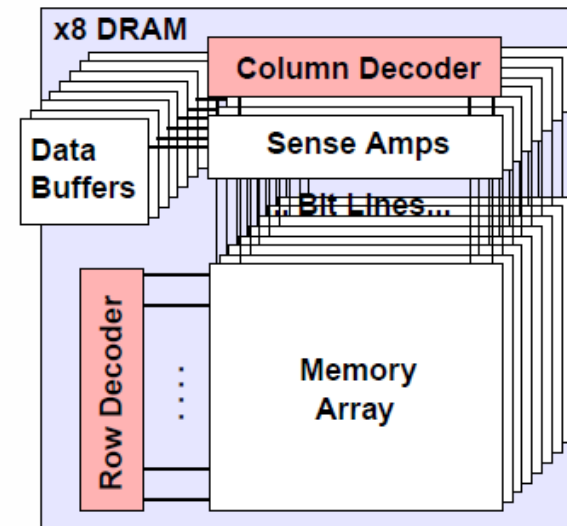

x8 DRAM

This is per bank. Typical DRAMs have 2+ banks

SRAM vs. DRAM

◆ SRAM

- Faster access using bit-differential sense
 - Pre-charging required
- Strong storage → doesn't need refreshing
- But, static power consumption due to V_{dd} to ground paths

◆ DRAM

- Smaller cells → higher density
 - Refreshing required
- But, dynamic power consumption due to refreshing



FLASH Solid-State Storage

FLASH Cell

Electrically modifiable, non-volatile storage

First developed by Toshiba around 1980

- ▣ Evolved from ROM and EEPROM devices

Principle of operation

- ▣ Transistor with a second “floating” gate
- ▣ Floating gate can trap electrons


- ▣ Results in detectable change in V_t

V_t = threshold voltage

= transistor turn-on point


→ High V_t → slow transistor

Low V_t → fast transistor

 


FLASH cell operation (case of NAND)

**Erasing
to logical “1”**

 

“Quantum tunneling”
Drains charge from FG

 
**Programming (=writing)
to logical “0”**



“Hot-electron injection”
traps charge in FG

FLASH cell operation (NAND)

Reading

 

Turn on low V_t or High V_t ?

Detect I_{on} to read 0 or 1

The strength of flow current between source and gate tells us its logical value : “1” or “0”

Value 1:

erased

=less resistant

=fast turn on

Value 0:

programmed

= strong resistance
(due to FTL electrons)

= slow turn on

Question?

Announcements

Reading: Finish reading Chapter 10!

Handouts